


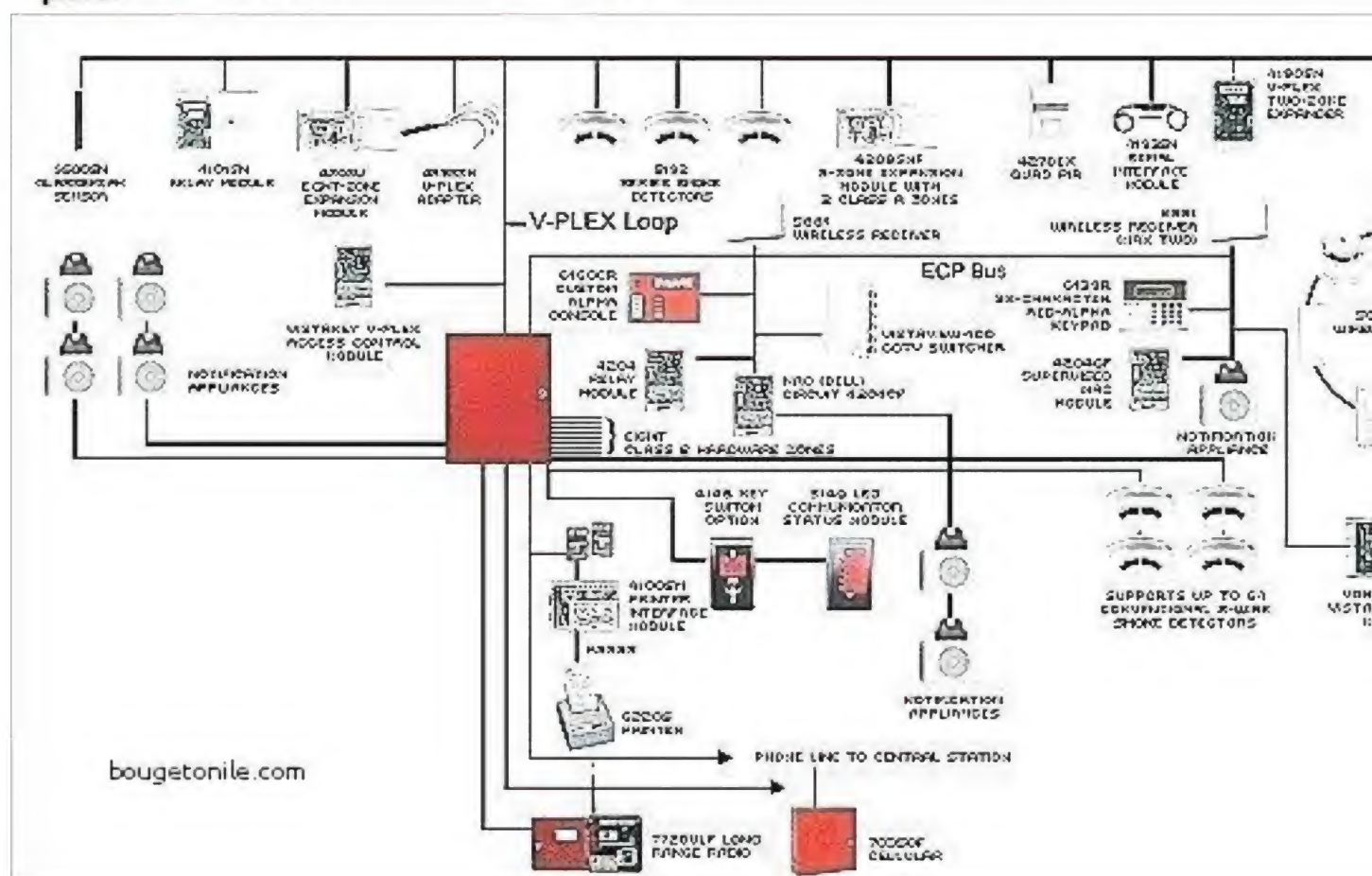
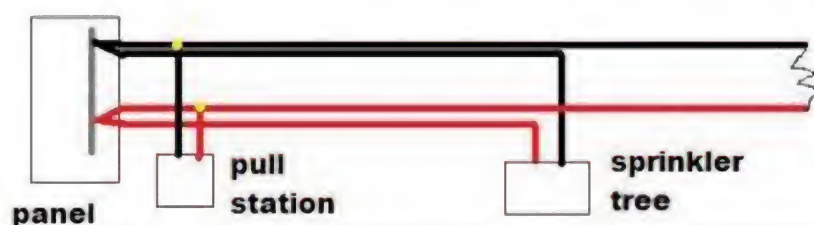
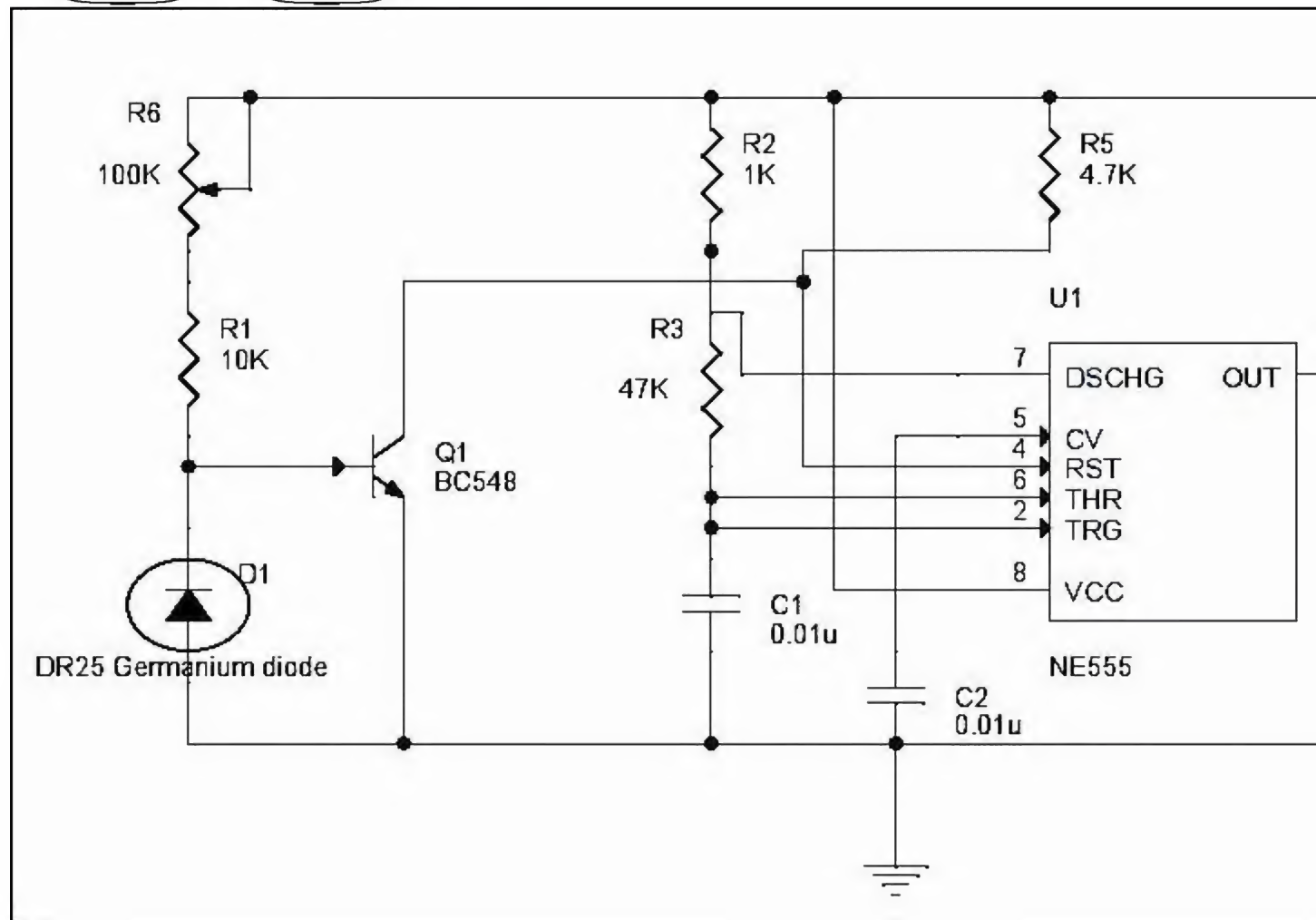


The diagram illustrates a fire alarm system layout. On the left, a box labeled "panel" is connected to a horizontal line. This line branches into two paths: a black line and a red line. The black line continues horizontally and has two vertical branches leading down to boxes labeled "pull station". The red line continues horizontally and has two vertical branches leading down to boxes labeled "sprinkler tree". The horizontal lines end in arrows pointing to the right, indicating the direction of signal flow.

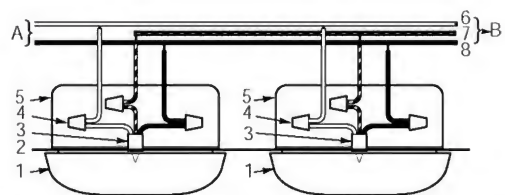

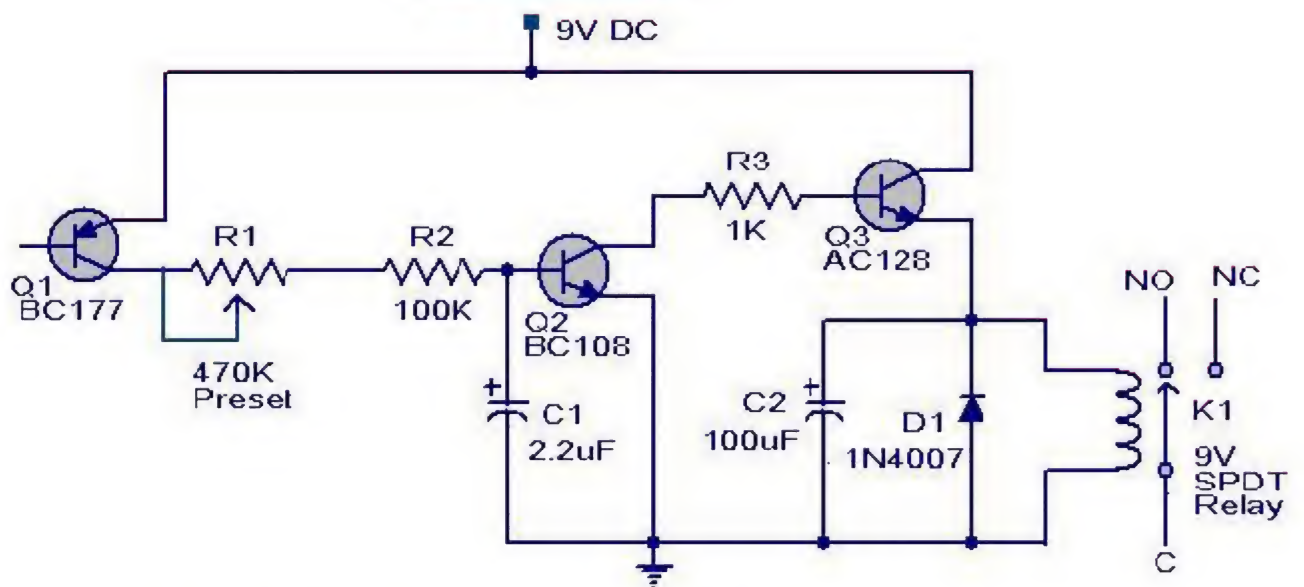

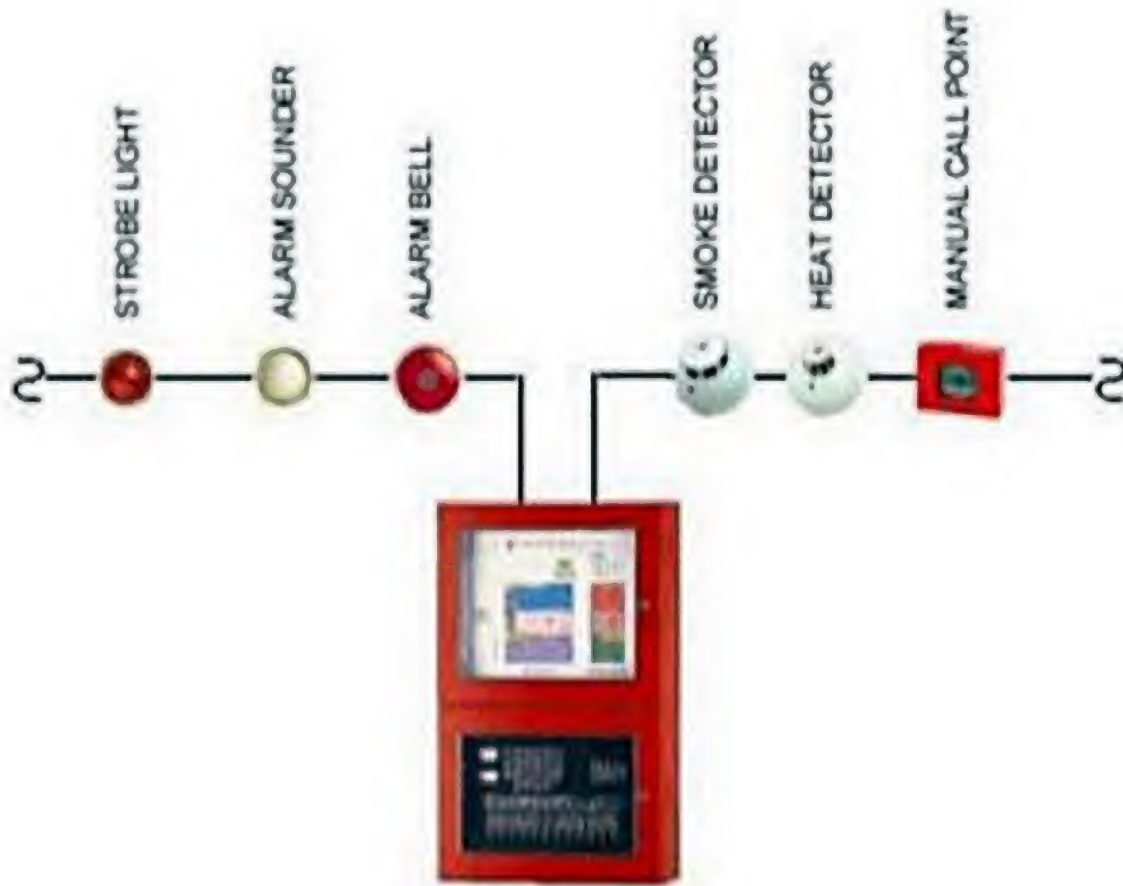

Low cost fire alarm circuit

[www.circuitstoday.com](http://www.circuitstoday.com)